

ECE159 Exam Review

QiLin Xue and Shem

April 21, 2021


Contents

1	DC Analysis	2
1.1	Voltage and Current Division	2
1.2	Mesh and Nodal Analysis	2
1.3	Superposition	2
1.4	Source Transformation	3
1.5	Thevenin Equivalent Circuit	3
1.6	Norton Equivalent Circuit	3
2	Operational Amplifiers	3
2.1	Ideal OP Amp	4
2.2	Types of Amplifiers	5
3	First Order Circuits	6
3.1	Overview of Capacitors and Inductors	6
3.2	Natural Response	7
3.3	Step Responses	7
4	AC Circuits	8
4.1	Interpreting Complex Numbers	8
4.2	Resonance and Filters	8
4.2.1	Magnitude Scaling	9
4.3	Power	9
4.3.1	Optimal Power	9
4.3.2	Power Factor	9
4.3.3	Power Factor Correction	10
4.3.4	Apparent and Effective Value	11
4.3.5	Random Things when Doing Practice	11

1 DC Analysis

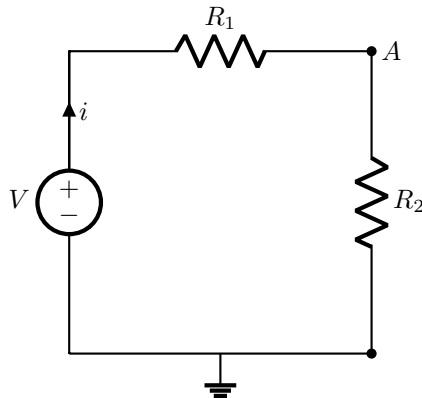1.1 Voltage and Current Division

For a series circuit, we can calculate the equivalent resistance by adding them.




For this circuit, we have:

$$R_{eq} = R_1 + R_2 \quad (1)$$

and the voltage is given by **voltage division**:

$$V_A = \frac{R_2}{R_1 + R_2} V \quad (2)$$

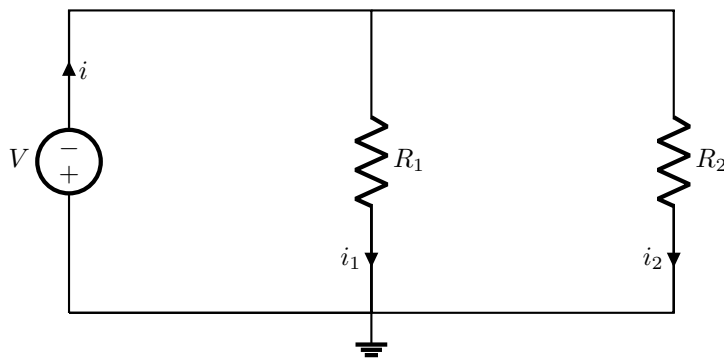For a parallel circuit, the effective resistance is the harmonic sum:



In this circuit, we have:

$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \frac{R_1 R_2}{R_1 + R_2} \quad (3)$$

and the current in the branches is given by **current division**:

$$i_1 = \frac{R_2}{R_1 + R_2} i \quad (4)$$

1.2 Mesh and Nodal Analysis

In mesh analysis, Kirchoff's Voltage law $\sum V = 0$ is written for each independent loop, and a system of equation is solved. The number of independent loops can be determined by finding the minimum number of wire cuts needed such that there are no loops.

In nodal analysis, we deal with the potentials at each node and write out Kirchoff's current law $\sum I = 0$ for the current *leaving* (or alternatively, entering) each node for each node where the voltage is unknown.

1.3 Superposition

Kirchoff's equations are linear. Each term includes only a first power of a current or a voltage, hence we can apply superposition. Let there be n independent voltage sources and m independent current sources. The current in the j^{th}


wire can be found as:

$$I_j = \sum_{k=1}^{n+m} I_j(k) \quad (5)$$

where $I_j(k)$ is the current in that wire when only the k^{th} battery (or current source) is included into the circuit. All other batteries are short circuited and all other current sources are removed by cutting off a connection wire. This same concept can be applied for voltage, but *not* power.

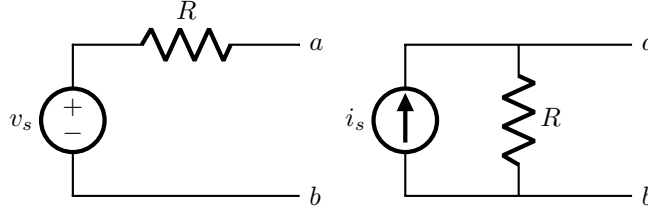1.4 Source Transformation

A source transformation is the process of replacing a voltage source v_s in series with a resistor R by a current source i_s in parallel with a resistor R , or vice versa. For example, these two circuits are equivalent:



where $v_s = i_s R$.

1.5 Thevenin Equivalent Circuit

Thevenin's Theorem tells us that any two-terminal circuit can be replaced by an equivalent voltage source V_{th} in series with a resistor R_{th} . These are related via:

$$R_{\text{th}} = \frac{V_{\text{th}}}{I_{\text{sc}}} \quad (6)$$

To calculate V_{th} , we find the *open circuit* voltage between the two terminals. To calculate R_{th} , there are three options:

1. Remove all independent voltage and current sources and calculate the equivalent resistance across the terminals.
2. Connect the two terminals via a wire with negligible resistance. Calculate the current I_{sc} through this wire and we can calculate R_{th} using equation 6.
3. Inject a test current I_{test} from one node, and measure the potential difference V_{test} . The resistance is then:


$$R_{\text{th}} = \frac{V_{\text{test}}}{I_{\text{test}}} \quad (7)$$

1.6 Norton Equivalent Circuit


Similar to Thevenin, we can also perform a source transformation such that we can replace any subcircuit element with an independent current source connected to a resistor in parallel. Note that calculating the equivalent resistance is done in the same way.

2 Operational Amplifiers

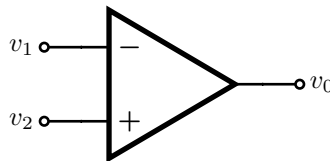An operational amplifier (op amp) is an active circuit element designed to perform mathematical operations of addition, subtraction, multiplication, division, differentiation, and integration.



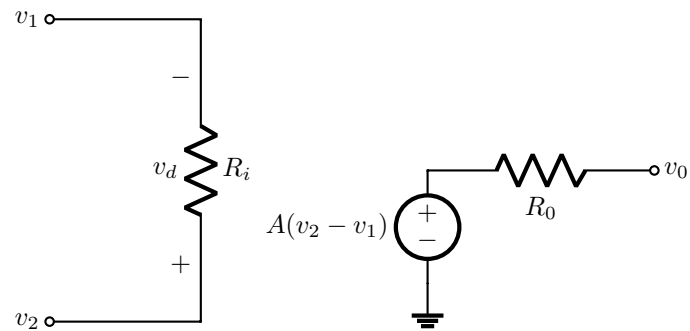It is equivalent to the following circuit:



where $A \gg 1$ is known as the open-loop voltage gain. The input resistance R_i is typically very big.

2.1 Ideal OP Amp

For an ideal OP Amp, we have an infinite open-loop gain, infinite input resistance, and zero output resistance. This gives the following results:


- The currents into both input terminals are zero.
- Voltage across input terminals are zero.

2.2 Types of Amplifiers

Here is a list of common amplifiers:


- Inverting Amplifier:

$$v_0 = -\frac{R_2}{R_1} v_i \quad (8)$$

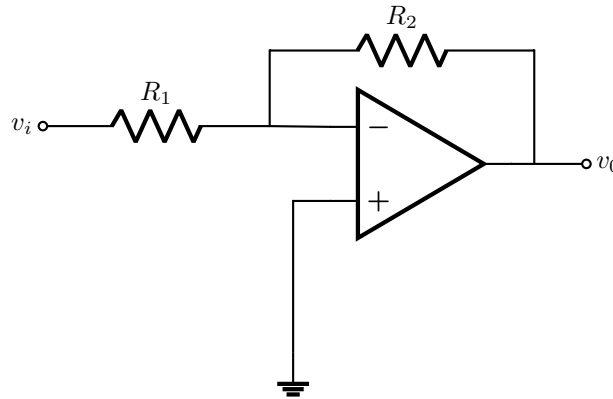


- Noninverting amplifier:
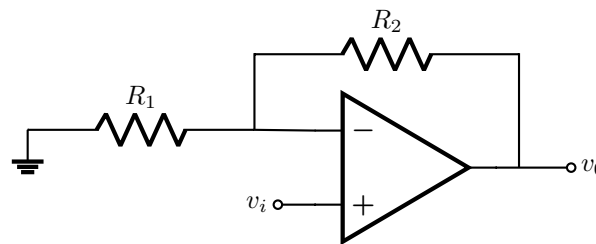
$$v_0 = \left(1 + \frac{R_2}{R_1}\right) v_i \quad (9)$$




- Voltage follower:

$$v_0 = v_i \quad (10)$$

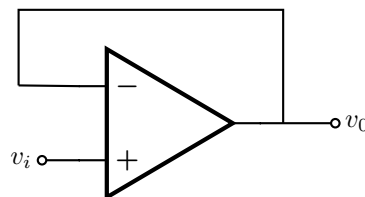


- Summer:
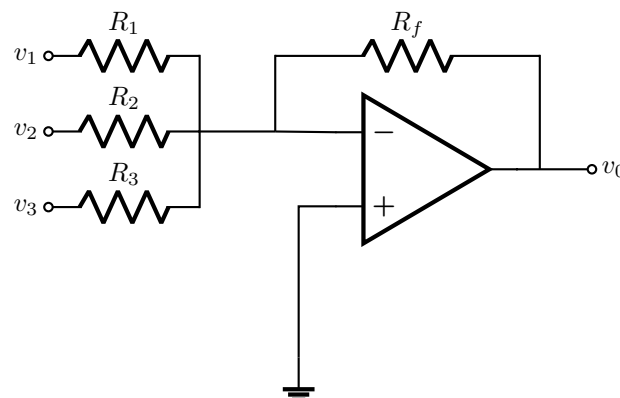
$$v_0 = -\left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3\right) \quad (11)$$



- Difference Amplifier:
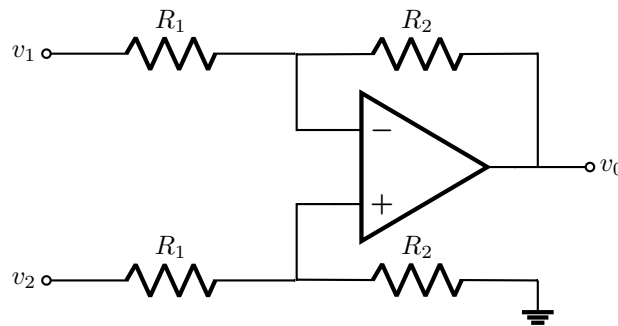
$$v_0 = \frac{R_2}{R_1}(v_2 - v_1) \quad (12)$$



3 First Order Circuits

3.1 Overview of Capacitors and Inductors

A capacitor is able to store charge such that the voltage across it is:

$$V = \frac{q}{C} \quad (13)$$

where C is the capacitance. Differentiating both sides, we have:

$$\frac{dV}{dt} = \frac{i}{C} \implies i = C \frac{dV}{dt} \quad (14)$$

Since the current cannot be infinite, the voltage across a capacitor must be differentiable (i.e. smooth). When multiple capacitors are in series, the equivalent capacitance is:

$$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots \right)^{-1} \quad (15)$$

For multiple capacitors in parallel, the equivalent capacitance is:

$$C_{eq} = C_1 + C_2 + \dots \quad (16)$$

The energy stored in a capacitor is given by:

$$U = \frac{q^2}{2C} = \frac{1}{2}CV^2 = \frac{q}{2V} \quad (17)$$

An inductor maintains a voltage that resists a change in current (i.e. via Lenz's Law). This means the voltage across a resistor is:

$$V = -L \frac{di}{dt} \quad (18)$$

where L is the inductance. Since the voltage across cannot be infinite, the current across it has to be differentiable. When inductors are added in series, the equivalent inductance is:

$$L_{eq} = L_1 + L_2 + \dots \quad (19)$$

and in parallel:

$$L_{eq} = \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots \right)^{-1} \quad (20)$$

The energy stored in an inductor is:

$$U = \frac{1}{2}Li^2 \quad (21)$$

Idea: For RL and RC circuits, at time scales much shorter than the characteristic times $\tau = RC$ or $\tau = L/R$ (i.e. right after a switch is opened), the capacitor's charge and inductor's current remain almost constant. In particular, if a capacitor was chargeless, its voltage remains almost zero (i.e. short circuit). If there was no current in an inductor, its current remains zero (i.e. inductor may be considered to be broken). If a capacitor had a charge Q corresponding to a voltage V_0 , its voltage remains essentially constant (i.e. it acts and can be substituted by a battery of voltage V). Similarly, if an inductor had a current I_0 , it can be substituted by a respective constant current source. If we try to forcefully break the current through an inductor by switching it off, a rapid fall of current I creates a huge voltage $-L \frac{dI}{dt}$ which usually leads to a spark at the switch.

At time scales much larger than the characteristic times, the situation is reversed: the inductor can be considered a short-circuiting wire, and capacitor as an insulator. This is because all the currents and voltages tend exponentially towards the equilibrium state so that the different from the equilibrium value $\Delta \propto e^{-t/\tau}$: the capacitor charge is almost constant, hence there is no current, and the inductor current is almost constant, hence no voltage.

3.2 Natural Response

Since resistors provide a “decaying response” (see the mechanical analogy section), it is expected that RC and RL circuits have a decaying exponential, when there are no voltage sources:

$$x(t) = x(0)e^{-t/\tau} \quad (22)$$

where $x(0)$ is the initial value of a quantity (current or voltage), and τ is the time constant. For RC circuits, we have $\tau = RC$ and for RL circuits, we have $\tau = L/R$. It is the characteristic time for which a certain quantity decreases by a factor of $\frac{1}{e}$. For an RC circuit, we can derive this from the equation:

$$i_c + i_r = 0 \implies C \frac{dV}{dt} + \frac{V}{r} = 0 \quad (23)$$

though I prefer working with Kirchoff's Voltage Law:

$$-\frac{dq}{dt}R - \frac{q}{C} = 0 \quad (24)$$

This is because we see a similar structure for the inductor:

$$-iR - L \frac{di}{dt} = 0 \quad (25)$$

Notice the connection between q , i , and $\frac{di}{dt}$. This is important when formulating the mathematics behind complex AC circuits later.

3.3 Step Responses

When we have a sudden change (i.e. a voltage or current source is added), the circuit may behave slightly differently. Since it is a first order circuit, we should still expect an exponential pattern. If we add a constant voltage or current term to the differential equation above, we can easily solve for it. Alternatively, we can abuse the fact that it is a linear differential equation so we can write the general solution as:

$$\text{complete response} = \text{natural response} + \text{forced response} \quad (26)$$

or

$$v = v_n + v_f \quad (27)$$

or:

$$v = v_t + v_{ss} \quad (28)$$

Here, v_t is the transient response, and it will die out with time. The steady state response v_{ss} is the behaviour of the circuit a long time after an external excitation is applied. As a result, we can write out the voltage of a capacitor:

$$\boxed{v(t) = v(\infty) + [v(0) - v(\infty)]e^{-t/\tau}} \quad (29)$$

Taking the derivative and rearranging:

$$i_c(t) = \frac{V_{th} - V(t_0)}{R_{th}} e^{-t/\tau} \quad (30)$$

and similarly for an RL circuit:

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau} \quad (31)$$

4 AC Circuits

In AC circuits, we may have combinations of inductors, capacitors, resistors, and sinusoidal voltage sources. We are concerned only with the steady state response. We can do this with phasors. Suppose the voltage frequency is ω , then the **impedances** are:

$$Z_R = R \quad (32)$$

$$Z_C = \frac{-j}{\omega C} = \frac{1}{j\omega C} \quad (33)$$

$$Z_L = j\omega L \quad (34)$$

where $j^2 = -1$ is the imaginary number. The **admittance** is the inverse of the impedance. Using these impedances, we can effectively “solve” an AC circuit in the same way that we solve a DC circuit.

4.1 Interpreting Complex Numbers

Note that we can convert between cartesian and polar forms of complex numbers via:

$$a + jb = r\angle\theta \quad (35)$$

where $r = \sqrt{a^2 + b^2}$ and $\tan\theta = \frac{b}{a}$. Suppose that the voltage is in the form of:

$$V = V_0\angle\theta \quad (36)$$

This simply means that the voltage is a sinusoidal wave with a magnitude of V_0 , and has a phase shift of θ , where the phase shift is calculated relative to some reference (usually the input voltage). We can interpret complex current in the same way.

4.2 Resonance and Filters

Resonance occurs when:

$$\omega_c = \frac{1}{\sqrt{LC}} \quad (37)$$

A filter is a circuit that is designed to pass signals with desired frequencies and reject or attenuate others. A **passive filter** consists of only passive elements R , L , and C . There are four different types of filters:

- Low-pass: passes low frequencies and stops high frequencies (i.e. RC)
- High-pass: passes high frequencies and stops low frequencies (i.e. CR)
- Band-Pass: Passes frequencies within a frequency band. (i.e. LCR)
- Band-stop: Passes frequencies outside a frequency band. (i.e. RCL)

The transfer function is defined as

$$H(\omega) = \frac{V_o}{V_i} \quad (38)$$

describes the increase/decrease in voltage at a given load. The transfer function for each filter at key frequencies are given below:

Type	$H(0)$	$H(\infty)$	$H(\omega_c)$
Low Pass	1	0	$\frac{1}{\sqrt{2}}$
High Pass	0	1	$\frac{1}{\sqrt{2}}$
Band Pass	0	0	1
Band Stop	1	1	0

4.2.1 Magnitude Scaling

In decibel scale, we define:

$$H_{\text{dB}} = 20 \log_{10} H \quad (39)$$

4.3 Power

Notation: I will use bolded variables to represent complex numbers: The most general power is the **complex power**:

$$\mathbf{S} = P + jQ \quad (40)$$

$$= \mathbf{V}_{\text{rms}} (\mathbf{I}_{\text{rms}})^* \quad (41)$$

$$= V_{\text{rms}} I_{\text{rms}} \angle(\theta_v - \theta_i) \quad (42)$$

$$= \frac{1}{2} \mathbf{V}_m \mathbf{I}_m^* \quad (43)$$

$$= \mathbf{Z} I_{\text{rms}}^2 \quad (44)$$

$$= \frac{V_{\text{rms}}^2}{\mathbf{Z}^*} \quad (45)$$

We will define $\theta = \theta_v - \theta_i$. Here, P is the **real power**:

$$P = S \cos(\theta_v - \theta_i) \quad (46)$$

and $S = \sqrt{P^2 + Q^2}$ is the **apparent power**. The **reactive power** is:

$$Q = S \sin(\theta_v - \theta_i) \quad (47)$$

4.3.1 Optimal Power

The optimal resistance and reactance of a load such that the maximum power is delivered to it in an AC circuit is given when:

$$R_L = \sqrt{R_{\text{th}}^2 + (X_{\text{th}} + X_L)^2} \quad (48)$$

$$X_L = -X_{\text{th}} \quad (49)$$

If both these criteria are satisfied, then:

$$P_{\text{max}} = \frac{|\mathbf{V}_{\text{th}}|^2}{8R_{\text{eq}}} \quad (50)$$

In general, the average power delivered to the load is

$$P = \frac{1}{2} |\mathbf{I}|^2 R_L = \frac{|\mathbf{V}_{\text{th}}|^2 R_L / 2}{(R_{\text{th}} + R_L)^2 + (X_{\text{th}} + X_L)^2} \quad (51)$$

Warning: Do not confuse this with the power delivered to a load in a DC circuit:

$$P = \frac{V_{\text{th}}^2}{4R_{\text{th}}} \quad (52)$$

the reason for the extra factor of $\frac{1}{2}$ in the AC circuit case, is that the power is a sinusoidal wave and we are looking for only the *average power*.

4.3.2 Power Factor

We can define the power factor to be:

$$\text{pf} = \cos \theta = \cos(\theta_v - \theta_i) \quad (53)$$

such that:

$$P = S \cdot \text{bf} \quad (54)$$

However, note that for each power factor, there are two possible values of θ that satisfy it. As a result, we define:

- **Leading pf:** $\theta < 0$
- **Lagging pf:** $\theta > 0$

Special cases:

- Resistor: $pf = 1$
- Inductor: $pf = 0$ lag
- Capacitor $pf = 0$ lead
- RL: $0 < pf < 1$ lag
- RC: $0 < pf < 1$ lead
- RLC: $0 < pf < 1$ lag or lead. Specifically, it depends on the sign of:

$$\omega L - \frac{1}{\omega C} \quad (55)$$

4.3.3 Power Factor Correction

The process of increasing the power factor without altering the voltage or current to the original load is known as power factor correction. It can be viewed as the addition of a reactive element (usually a capacitor) in parallel with an inductive load in order to make the power factor closer to unity.

An inductive load is modeled as a series combination of an inductor and a resistor.

The value of the required shunt capacitance C is determine to be:


$$C = \frac{P(\tan \theta_1 - \tan \theta_2)}{\omega V_{\text{rms}}^2} \quad (56)$$

where θ_1 is the initial power factor angle and θ_2 is the final angle. This equation is derived from the following principles.

- We want the real power P to be constant.
- We want to change the power factor, which depends solely on the power factor angle. As a result, we can only change the imaginary part Q .
- To do so, we need to figure out how much of the imaginary power do we want to increase/decrease, and then perform phasor math (and using impedances) to figure out the capacitance C necessary to do so. Specifically, if we need to increase the reactance by Q_C to achieve the desired pf, we select the capacitance:

$$X_c = \frac{V_{\text{rms}}^2}{Q_c} \quad \text{or} \quad C = -\frac{Q_c}{\omega V_{\text{rms}}^2} \quad (57)$$

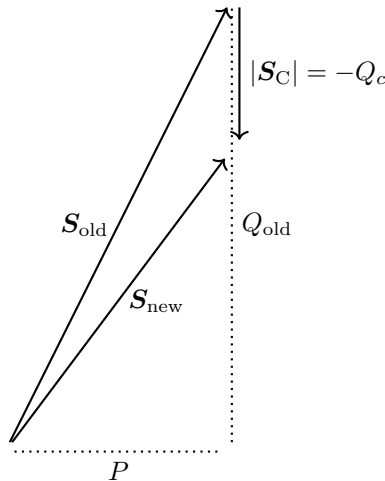We can draw a power triangle to illustrate this:



From this, note that:

$$\mathbf{S}_{\text{old}} + \mathbf{S}_C = \mathbf{S}_{\text{new}} \quad (58)$$

so we can define (note that we defined Q_C is a negative quantity here):

$$Q_{\text{new}} = Q_{\text{old}} + Q_c \quad (59)$$

which gives:

$$\frac{Q}{P} = \tan \theta_{\text{old}} \quad (60)$$

and:

$$\frac{Q_{\text{new}}}{P} = \tan \theta_{\text{new}} \quad (61)$$

To make the power factor unity, we set $Q_C = -Q_L$ where Q_L is the reactance of the load.

4.3.4 Apparent and Effective Value

The effective value of a periodic current is the DC current that delivers the same average power to a resistor as the periodic current:

$$I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} \quad (62)$$

for an arbitrary periodic function $x(t)$, the effective (or **root mean square** value) is:

$$X_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T x^2 dt} \quad (63)$$

We can convert between the rms value and the peak values of a sinusoidal function:

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}, \quad I_{\text{rms}} = \frac{I_m}{\sqrt{2}} \quad (64)$$

4.3.5 Random Things when Doing Practice

- $|\mathbf{S}|$ and $|\mathbf{Z}|$ are scalar multiples of each other. As a result, \mathbf{S} has the same power factor angle as \mathbf{Z} : $\mathbf{S} = \mathbf{Z}I_{\text{rms}}^2$.
- The angular frequency is not the same as frequency:

$$\omega = 2\pi f \quad (65)$$

This conversion factor also works if we are working with complex voltages.